
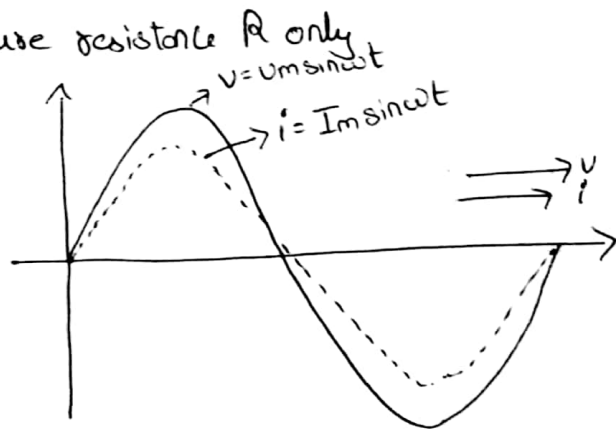


- The path for the flow of alternating current is called AC circuits
- In a DC circuit the current flowing through circuit is given by $I = \frac{V}{R}$
- However in AC circuit voltage and current changes from instant to instant and so give rise to magnetic (inductive) and electrostatic (capacitive) effects
- So in an AC circuit inductance and capacitance must be considered in addition to resistor

AC Circuit containing pure ohmic Resistance :-

- When alternating voltage is applied across a pure ohmic resistance current flows in one direction during 1st $\frac{1}{2}$ cycle and opposite direction in next $\frac{1}{2}$ cycle thus constituting alternating current in circuit.

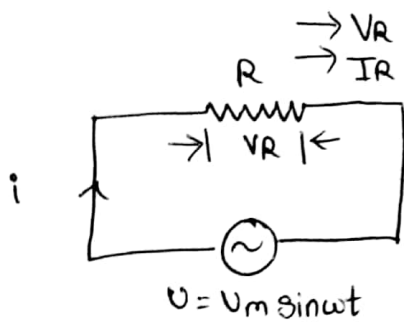Let us consider an AC circuit with pure resistance R only



Let the applied voltage be given by the Eqn

$$V = V_m \sin \omega t$$

$$V = V_m \sin \omega t \rightarrow \text{①}$$

as a result of this alternating voltage and alternating current will flow through circuit
The applied voltage has its supply the drop in resistance

$$V = iR$$

Substituting value of V in Eqn ①

$$iR = V_m \sin \omega t$$

$$i = \frac{V_m}{R} \sin \omega t \quad \left[\text{The value of } i \text{ is maximum when } \sin \omega t = 1 \right] \rightarrow \text{②}$$

$$I_m = \frac{V_m}{R}$$

Eqn ② becomes $i = I_m \sin \omega t$

From Eqn ① & ② it is apparent that voltage and current are in phase with each other. This is indicated by co-axial & vector diagram.

Inductive
Resistor
Capacitive

Power:- voltage and current are changing at every instant

$$\begin{aligned} \text{Instantaneous power} - P &= V I \\ &= V_m \sin \omega t \cdot I_m \sin \omega t \\ &= V_m I_m \sin^2 \omega t \\ &= V_m I_m \frac{(1 - \cos 2\omega t)}{2} \\ &= \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t \end{aligned}$$

instantaneous part consist of

$$\text{constant part} = \frac{V_m I_m}{2}$$

Fluctuating part = $\frac{V_m I_m}{2} \cos 2\omega t$ of frequency double that of voltage and current wave

The average value of $\frac{V_m I_m}{2} \cos 2\omega t$ over complete cycle is zero.


hence power for complete cycle is $P = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} =$

$$P = VI \text{ watts}$$

where $V =$ rms value of applied voltage
 $I =$ rms value of current.

Power Curve:-

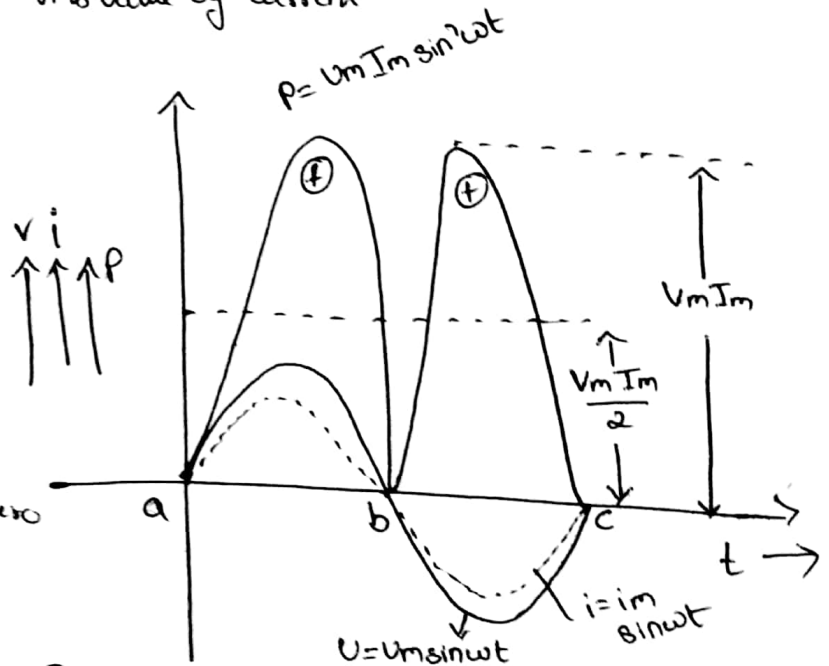- power curve for purely resistive CRT is shown
- It is apparent that power in such circuit is zero
- only at the instant a, b, and c when both voltage & current are zero
- but its positive at all other instant




- In other words power is always (+)ve so that power is always lost in resistive AC circuit.
- The power is dissipated as heat.

A.C Circuit Containing pure Inductance :-

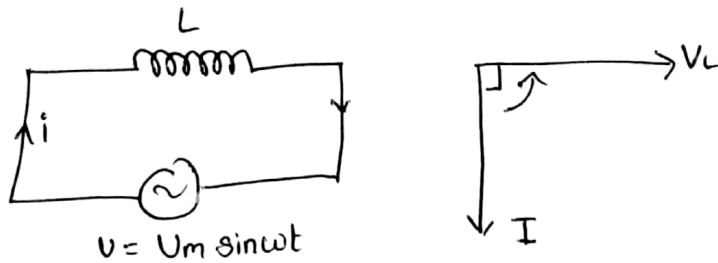(2)

Inductive coil is a coil with or without an iron core and negligible resistance. However a coil of thick copper wire wound on a laminated iron core has negligible resistance.

For the purpose of our study we will consider purely inductive coil.



- When ever alternating voltage is applied to a circuit containing a pure inductance
- the back EMF is produced because of self inductance of the coil
- This back EMF oppose the rise and fall of current at every stage.
- Because of absence of voltage drop, applied voltage has to overcome this self-induced EMF.

let the applied voltage be $v = V_m \sin \omega t$
 self inductance of coil = L henry

self induced e.m.f in the coil $e_L = -L \frac{di}{dt}$

since applied voltage at every instant is equal and opposite to self-inductance e.m.f i.e. $v = -e_L$

$$V_m \sin \omega t = - \left(-L \frac{di}{dt} \right)$$

$$di = \frac{V_m}{L} \sin \omega t dt$$

on integrating b.s we get

$$\int di = \int \frac{V_m}{L} \sin \omega t dt$$

$$i = \frac{V_m}{L} \int \sin \omega t dt$$

$$i = \frac{V_m}{\omega L} (-\cos \omega t) + A$$

$v = -e_L$
 But $v = V_m \sin \omega t$
 $V_m \sin \omega t = - \left(-L \frac{di}{dt} \right)$

$$-L di = V_m \sin \omega t dt$$

$$di = \frac{V_m}{L} \sin \omega t dt$$

$$\int di = \int \frac{V_m}{L} \sin \omega t dt$$

$$i = \frac{V_m}{\omega L} (-\cos \omega t) + A$$

Where A is a constant of integration which is found to be zero
 From initial condition.


$$i = -\frac{V_m}{\omega L} \cos \omega t$$

$$i = \frac{V_m}{\omega L} \sin \left(\omega t - \frac{\pi}{2} \right)$$

- The current will be max when $\sin \left(\omega t - \frac{\pi}{2} \right) = 1$
- hence value of max current $I_m = \frac{V_m}{\omega L}$
- and instantaneous current may be expressed as $i = I_m \sin \left(\omega t - \frac{\pi}{2} \right)$

Current will be maximum when $\sin \left(\omega t - \frac{\pi}{2} \right) = 1$
 hence value of maximum current $I_m = \frac{V_m}{\omega L}$

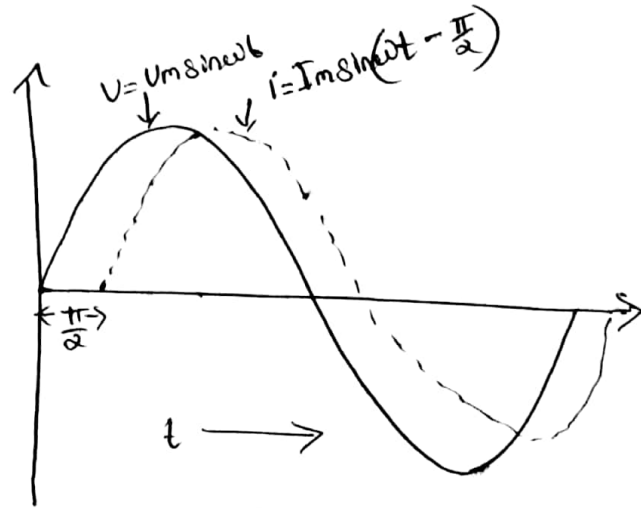- From the expression of instantaneous applied voltage $V = V_m \sin \omega t$ and instantaneous current flowing through a purely inductive coil
- It is clear that current lags behind voltage by $\frac{\pi}{2}$



Inductive Reactance :-

$$\omega L$$

In expression $I_m = \frac{V_m}{\omega L}$ is known as inductive reactance denoted by X_L

unit of L = henry

ω = radians/sec

X_L = ohms

$$X_L = \omega L$$

$$X_L = 2\pi f L$$

hence inductive reactance plays the part of resistance

Power :- Instantaneous power :-


$$\begin{aligned} P &= v \times i \\ &= V_m \sin \omega t \cdot I_m \sin \left(\omega t - \frac{\pi}{2} \right) \\ &= -V_m I_m \sin \omega t \cos \omega t \\ &= -\frac{V_m I_m}{2} \sin 2\omega t \end{aligned}$$

Power measured by a wattmeter is average value of p which is zero
i.e. average of a sinusoidal quantity of double frequency over a complete cycle
is put this in mathematical terms.

over for whole cycle
$$P = -\frac{V_m I_m}{2} \int_0^{2\pi} \sin 2\omega t dt = 0$$

hence power absorbed in pure inductive circuit is zero.



Power Curve :-

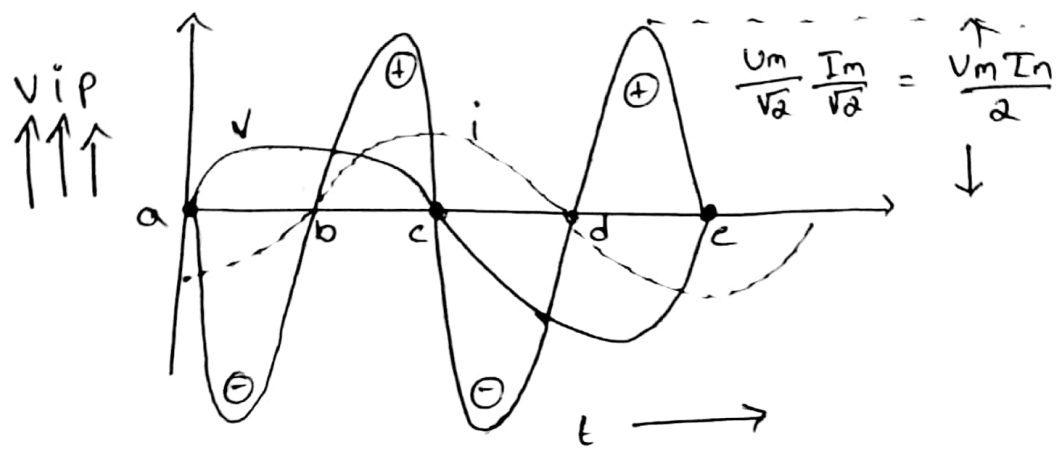

- Power Curve for pure inductive circuit is shown
 - This indicates that power absorbed in the circuit is zero
 - at the instant a, c and e voltage is zero. hence power is zero.
 - when current is at b and d power is also zero
 - Between a and b voltage and current are in opposite direction
 - Between b and c voltage and current are in same direction
 - Between c and d power is negative and energy is taken from the circuit
 - Between d and e power is positive and energy is put in the circuit
- hence net power is zero

R.C Circuit Containing Pure Capacitance:-

(1)

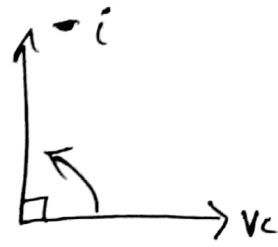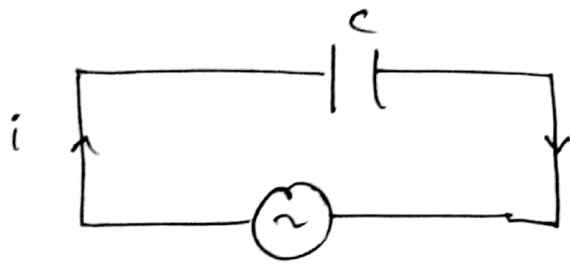

$$u = V_m \sin \omega t$$

- When an alternating voltage is applied across the plates of a capacitor
- Capacitor is charged in one direction and then in opposite direction as the voltage reverses.
- Let alternating voltage represented by $u = V_m \sin \omega t$ applied across the capacitor of capacitance C Farads.

Instantaneous Charge $q = CV$
 $= C V_m \sin \omega t$

Capacitor current is equal to rate of change of charge

$$i = \frac{dq}{dt} = \frac{d[C V_m \sin \omega t]}{dt}$$

$$= \omega C V_m \cos \omega t$$

$$i = \frac{V_m}{\frac{1}{\omega C}} \cos \omega t$$

$$i = \frac{V_m}{\frac{1}{\omega C}} \sin \left(\omega t + \frac{\pi}{2} \right) \rightarrow \text{①}$$

The current is maximum when $t=0$

$$I_m = \frac{V_m}{\frac{1}{\omega C}} \rightarrow \text{②}$$

Substituting Eqn ② in Eq ①

$$i = I_m \sin \left(\omega t + \frac{\pi}{2} \right)$$


Capacitive Reactance :- $\frac{1}{\omega C}$ in the Expression

$I_m = \frac{V_m}{\frac{1}{\omega C}}$ is known as Capacitive Reactance and

Denoted by X_c i.e. $X_c = \frac{1}{\omega C}$

Where unit of $C = \text{Farad}$
 $\omega = \text{radians}$
 $X_c = \text{ohms}$

1 henry

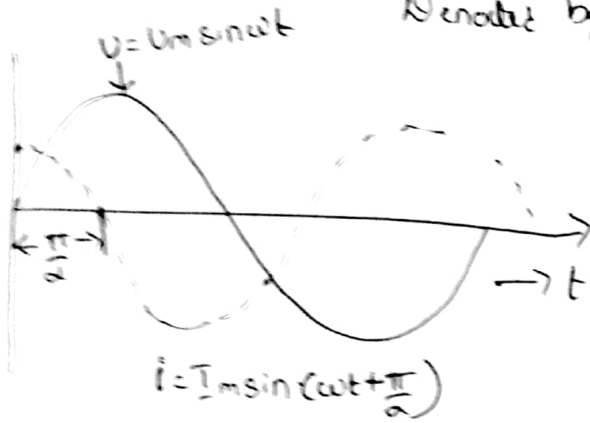

- here applied voltage $V = V_m \sin \omega t$
- Current $i = I_m \sin (\omega t + \frac{\pi}{2})$
- Current in pure capacitor leads the voltage by quarter cycle
- Phase difference b/w voltage & current is $\frac{\pi}{2}$, with current leading

Power :- Instantaneous power

$$P = Vi$$

$$= V_m \sin \omega t \cdot I_m \sin (\omega t + \frac{\pi}{2})$$

$$= V_m I_m \sin \omega t \cos \omega t$$


$$= \frac{1}{2} V_m I_m \sin 2\omega t$$

Power for complete cycle = $\frac{1}{2} V_m I_m \int_0^{2\pi} \sin 2\omega t dt = 0$

"Average power consumed by pure capacitor is zero"


Power Curves :-

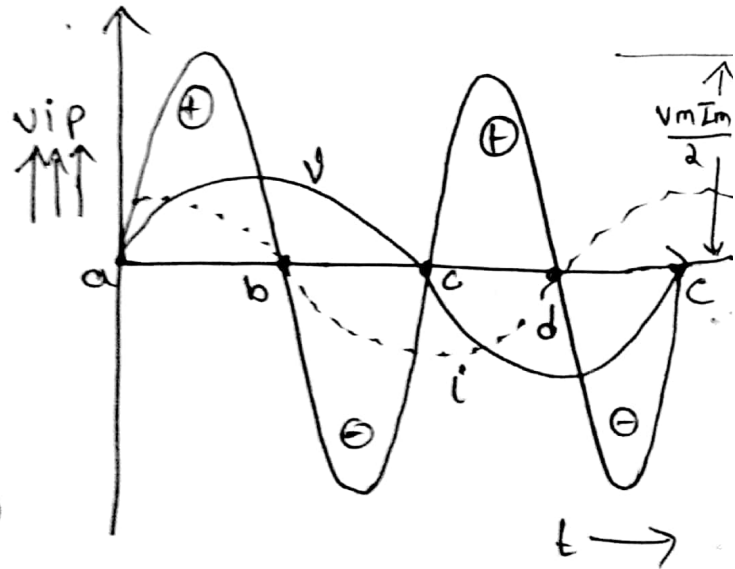- at instant b, d current is zero hence power is zero
- at instant a, c, e voltage is zero
- b/w a & b voltage & current are in same direction hence power is +ve power is put back into circuit
- b/w b & c voltage & current are in opposite direction hence power is -ve power is taken from circuit
- same b/w c & d and d & e



2 of 100 R-L Circuit :-


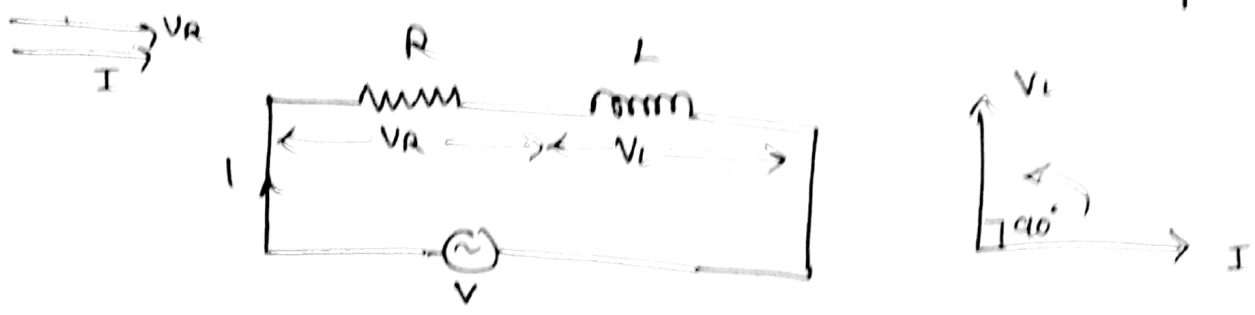
Consider an a.c circuit containing pure resistance "R" ohms and pure inductance L henry as shown



Let $V =$ r.m.s value of applied voltage
 $I =$ r.m.s value of the current

Voltage drop across Resistance $V_R = IR$ [voltage in phase with I]
 Voltage drop across inductance $V_L = IX_L$ [leading I by 90°]

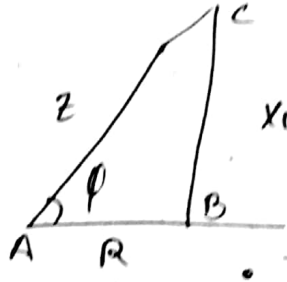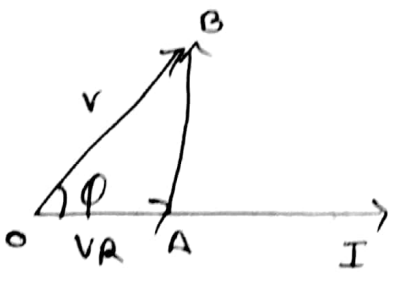The voltage drop across these two circuit components are shown in the figure



- Vector OA indicates V_R
- Vector AB indicates V_L
- The applied voltage V is the vector sum of two

$$V = \sqrt{V_R^2 + V_L^2}$$

$$= \sqrt{(IR)^2 + (IX_L)^2}$$

$$= I \sqrt{R^2 + X_L^2}$$


$$I = \frac{V}{\sqrt{R^2 + X_L^2}} \quad [\because \text{The term } \sqrt{R^2 + X_L^2} \text{ offers opposition for flow of current is called impedance}]$$

$$I = \frac{V}{Z}$$

Regarding the impedance triangle

$$Z^2 = R^2 + X_L^2$$
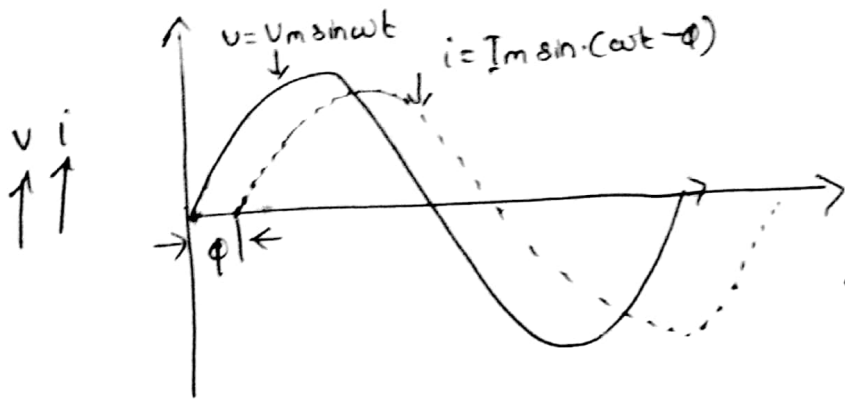
$$(\text{impedance})^2 = (\text{Resistance})^2 + (\text{reactance})^2$$



• applied voltage V leads the current I by angle ϕ

• $\tan \phi = \frac{V_L}{V_R} = \frac{I X_L}{I \cdot R} = \frac{X_L}{R}$
 = $\frac{\text{reactance}}{\text{resistance}}$

• From the wave form we observe that current lags behind applied voltage by angle " ϕ "


$\phi = \tan^{-1} \frac{X_L}{R}$

• If applied voltage is expressed as $V = V_m \sin \omega t$ and current is expressed as $i = I_m \sin(\omega t - \phi)$

where $I_m = \frac{V_m}{Z}$

Real power, Reactive power, apparent power and power factor

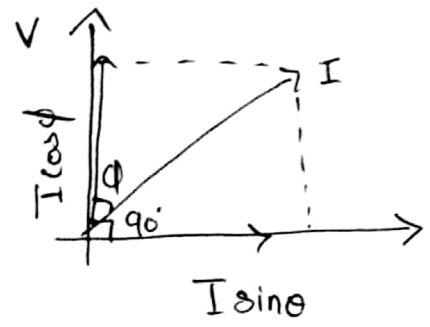• Consider a series R-L circuit drawing a current I (rms value) when alternating voltage V (rms value) is applied to it. Suppose the current lags behind the applied voltage by angle ϕ



* Power factor and its significance :-

"Power factor is the cosine of angle of lead or lag"

the angle of lag is shown in above fig hence power factor $\cos \phi$

addition to having numerical value.

- The power factor of circuit carries a notation that signifies the nature of circuit
- Neither equivalent circuit is resistive, inductive or capacitive
- Thus the power factor might be expressed as 0.8 lagging
- The lagging and leading refers to the phase of current vectors with voltage vectors.
- lagging power factor means current lags the voltage and circuit is inductive in nature
- leading power factor the current leads the voltage and circuit is capacitive in nature

Apparent power:- The product of Rms value of current & voltage is called apparent power

- Measured in terms of volt ampere (VA) or
- kilo volt ampere (kVA)

Real power :- The product of apparent power and power factor is called real power

- Expressed in watts or
- kilo watts "kW"

$$\text{Real power} = \text{volt ampere} \times \text{Power factor}$$

"W" "VA" "cos φ"

$$\text{Watts} = \text{VA} \cos \phi$$

It should be noted that power is only consumed by ohmic resistance only as pure inductor does not consume any power

$$P = VI \cos \phi$$

$$\cos \phi = \frac{R}{Z}$$

$$P = VI \cos \phi$$

$$= VI \times \frac{R}{Z}$$

$$= \sqrt{I} \times R \frac{I}{\sqrt{I}}$$

But $Z = \frac{V}{I}$


$$P = I^2 R \text{ watts}$$

Wage Power

Reactive power:- It is the power developed in the inductive reactance of the circuit

The quantity $VI \sin$ is called reactive power
it is measured in reactive volt-amperes or (VAR)

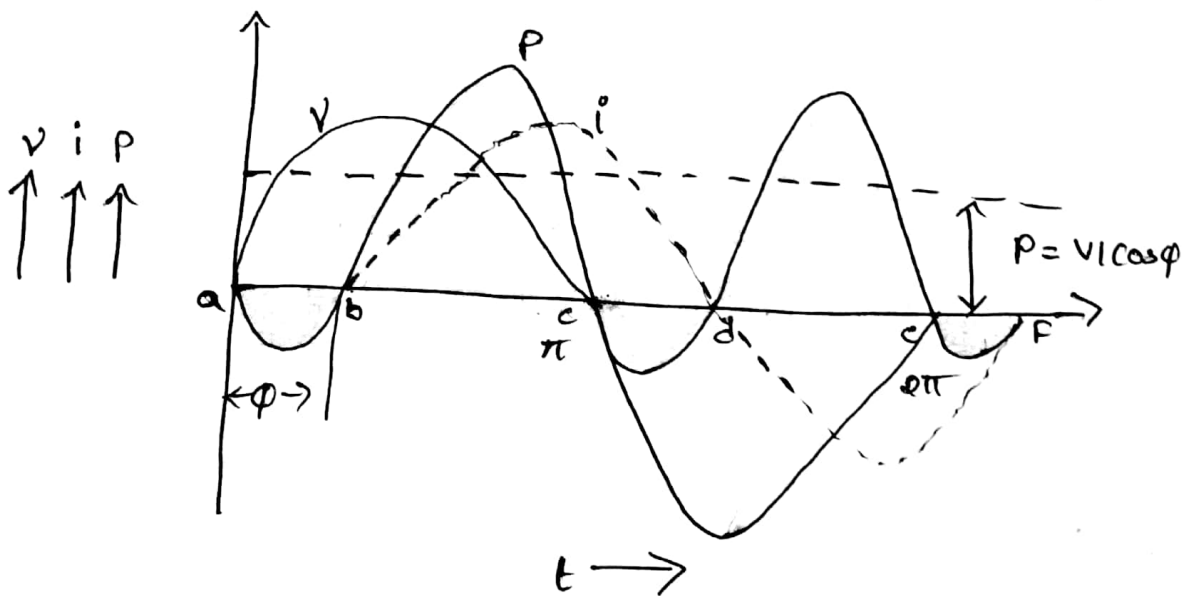The power consumed can be represented by means of wave form



instantaneous power

$$\begin{aligned}
 p &= vi \\
 &= V_m \sin \omega t \times I_m \sin(\omega t - \phi) \\
 &= V_m I_m \sin \omega t \sin(\omega t - \phi) \\
 &= \frac{1}{2} V_m I_m [\cos \phi - \cos(2\omega t - \phi)]
 \end{aligned}$$

The power consist of two parts :-

1. Constant part :- $\frac{1}{2} V_m I_m \cos \phi$
2. Sinusoidally varying part $\frac{1}{2} V_m I_m \cos(2\omega t - \phi)$
 - Frequency is double of voltage and current
 - average value over complete cycle is zero

average power consumed $P = \frac{1}{2} V_m I_m \cos \phi$

$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$$




$$P = VI \cos \phi$$

Where V & I are r.m.s values.

Power Curve :-

- From the curve greater part is \oplus ve and smaller part is \ominus ve so that the net power over the cycle is \oplus ve
- During time interval "a to b" applied voltage & current are in opposite direction hence power is negative
Under such condition inductor L returns power to circuit
- During time interval "b to c" applied voltage & current are in same direction hence power is positive
under such condition power is put in the circuit
- in the similar way at instant "c to d" inductor L returns power to circuit and at instant "d to e" power is put in the circuit
- The power absorbed by resistance R is converted in the heat and not returned.

Series R-C circuit :-

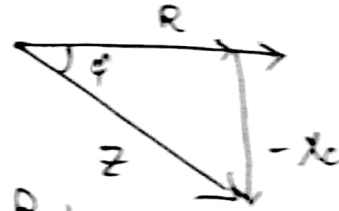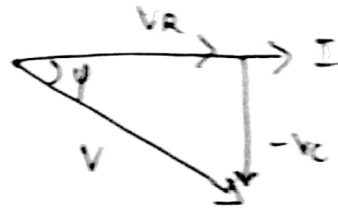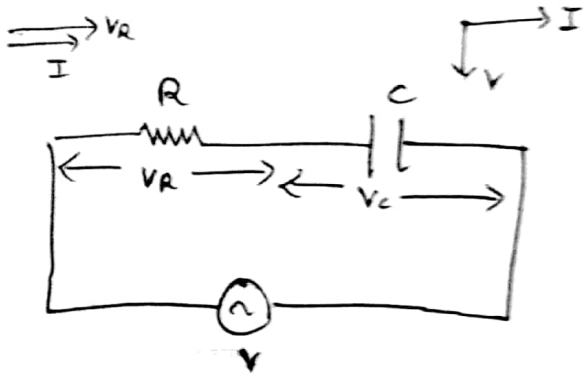

- Consider an ac circuit consist of resistance R ohms
capacitance C Farads

let $V =$ rms value of voltage
 $I =$ rms value of current

Voltage drop across resistance :- $V_R = IR$

Voltage drop across Capacitor :- $V_C = IX_C$

The Capacitive Reactance is negative so V_C is in negative direction of V across which is shown in above vector diagram

$$\text{we have } V = \sqrt{V_R^2 + (-V_C)^2}$$


$$= \sqrt{(IR)^2 + (-IX_C)^2}$$

$$V = I\sqrt{R^2 + X_C^2}$$

$$I = \frac{V}{\sqrt{R^2 + X_C^2}} = \frac{V}{Z}$$

The denominator in above Eqn is impedance of circuit $Z = \sqrt{R^2 + X_C^2}$
which depicts impedance triangle
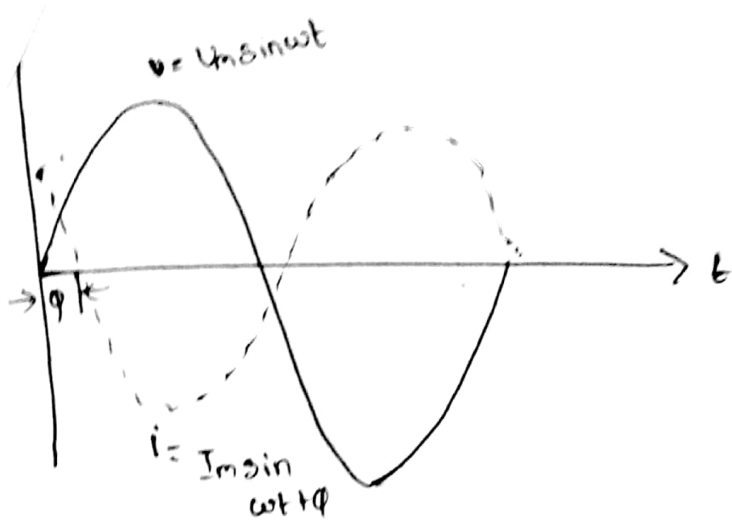
$$\text{Power factor } \Rightarrow \cos\phi = \frac{R}{Z}$$




- This implies that if the alternating voltage is $v = V_m \sin \omega t$
- The resultant alternating current in R-C circuit is $I = I_m \sin \omega t + \phi$
- Such that current leads the voltage by an angle ϕ

Power : Average power $P = v \times i$
 $= VI \cos \phi$


Power Curve :- The power curve for R-C series circuit is shown in below figure

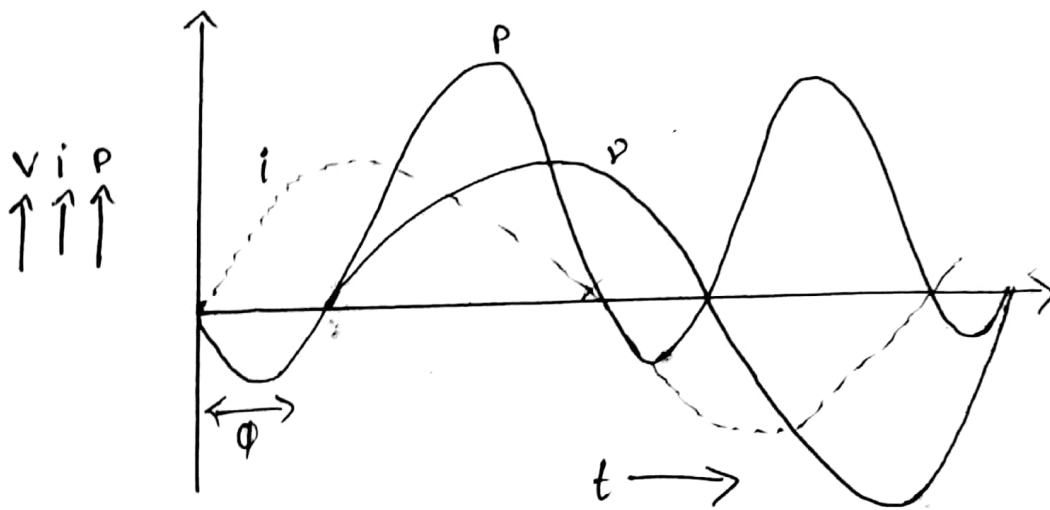- The curve indicates that the greater part is positive and the smaller part is negative
- So that net power is positive




Resistance, Inductance and Capacitance in Series :-

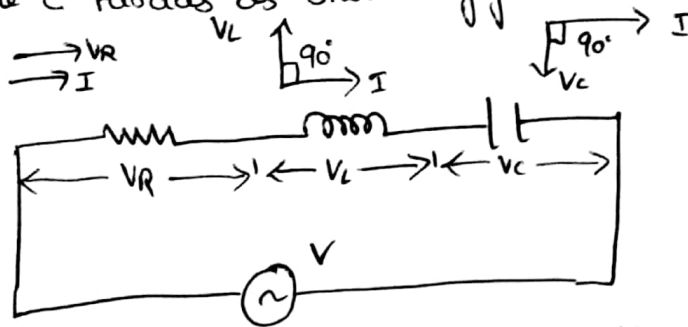Consider an AC series circuit containing resistance R ohms, inductance L henries and capacitance C farads as shown in figure.



V = r.m.s value of applied voltage
 I = r.m.s value of applied current

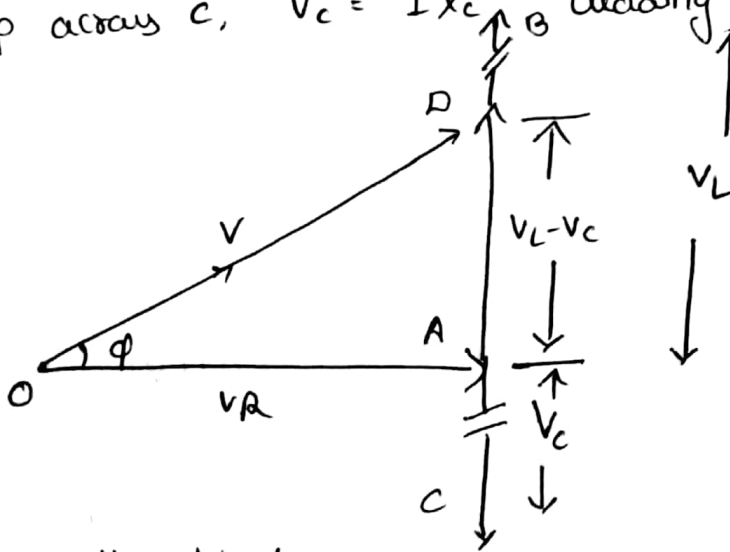Voltage drop across R , $V_R = IR$ "in phase with I "
 Voltage drop across L , $V_L = I \cdot X_L$ "leading I by 90° "
 Voltage drop across C , $V_C = I X_C$ "leading I by 90° "



in the above voltage triangle

$OA = V_R$
 $AB = V_L$
 $AC = V_C$

Thus the net reactive drop across the combination is

$$\begin{aligned}
 AD &= AB - AC && [O-A-C = B-D] \\
 &= AB - BD \\
 &= V_L - V_C \\
 &= I X_L - I X_C \\
 &= I (X_L - X_C)
 \end{aligned}$$

OD represent applied voltage V
it is the vector sum of OA and AD

$$OD = \sqrt{OA^2 + AD^2}$$

$$V = \sqrt{VR^2 + (IX_L - IX_C)^2}$$

$$V = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$= I \sqrt{R^2 + (X_L - X_C)^2}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$I = \frac{V}{\sqrt{R^2 + X^2}} = \frac{V}{Z}$$

The denominator $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + X^2}$ is impedance of circuit
where $X = \text{net reactance}$

- Phase angle $\phi := \tan^{-1} \left(\frac{X_L - X_C}{R} \right) \Rightarrow \frac{X}{R} \tan^{-1} \left(\frac{X}{R} \right)$
- Power factor $\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{R}{\sqrt{R^2 + X^2}}$
- power = $VI \cos \phi$

If applied voltage is represented by an Eqn $V = V_m \sin \omega t$
then resultant current in an R-L-C circuit is given by

$$i = I_m \sin(\omega t \pm \phi)$$

- If $X_C > X_L$; then current leads; (+)ve sign should be used
- If $X_L > X_C$; then current lags; (-)ve sign should be used

In any case current leads or lags the supply voltage by an angle ϕ

i.e $\tan \phi = \left[\frac{X}{R} \right]$

we employ the j operator then we have


$$Z = R + j(X_L - X_C)$$

Value of impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{Phase angle } \phi = \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$$
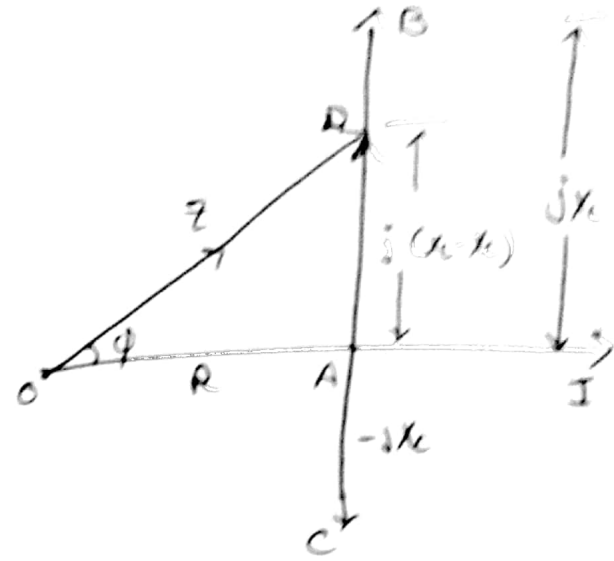
$$Z \angle \phi = Z \angle \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$$



Parallel AC Circuits :-


- In parallel a.c circuit voltage across each branch of circuit will be same
- Current in each branch depends upon the branch impedance
- Sine alternating currents are vector quantities.
- Total line current is the vector sum of branch current.

The Following are the 3 Methods used to solve parallel AC circuits


- Vector Method
- Admittance Method
- Symbolic or j -Method

* Vector Method :-

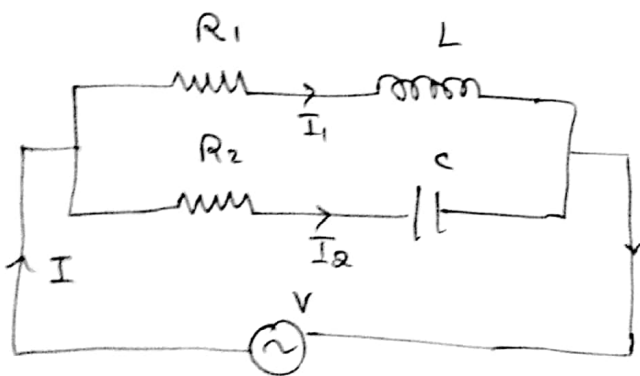- In this method line current is found by drawing the vector diagram of circuit
- A S voltage is common / same in parallel circuit hence it is taken as reference vector
- Various branch currents are represented vectorially
- Total line current can be determined from the vector diagram either by the parallelogram method or by method of components



- Let us take parallel a.c circuit which consisting of two branch impedance $Z_1 (R_1, L)$ and $Z_2 (R_2, C)$ connected in parallel across alternating voltage V volts
- The total current draw is vector sum of both current I_1 & I_2

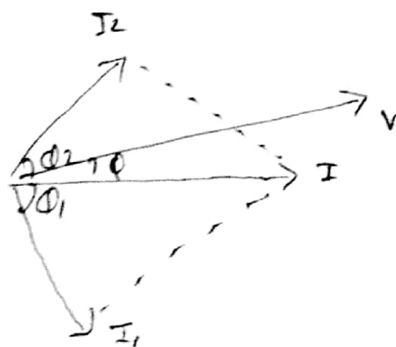

Branch 1:- Impedance $Z_1 = \sqrt{R_1^2 + X_L^2}$

$$\text{Current } I_1 = \frac{V}{Z_1}$$

$$\cos\phi_1 = \frac{R_1}{Z_1} \quad \text{or} \quad \phi_1 = \cos^{-1}\left[\frac{R_1}{Z_1}\right]$$

Current I_1 lags behind the applied voltage by ϕ_1

Branch 2:- Impedance $Z_2 = \sqrt{R_2^2 + X_C^2}$



$$\text{Current } I_2 = \frac{V}{Z_2}$$

$$\cos\phi_2 = \frac{R_2}{Z_2} \quad \text{or} \quad \phi_2 = \cos^{-1}\left[\frac{R_2}{Z_2}\right]$$

Current I_2 leads the applied voltage by ϕ_2

Resultant Current :- The total line current I is vector sum of branch current I_1 and I_2 which is found by draw a parallelogram

- The second method is the Method of Components i.e. resolving the branch current I_1 and I_2 along X-axis and Y-axis then finding the resultant of these components.
- Let the resultant current I and ϕ be the phase angle. Then the components of I along X-axis is equal to algebraic sum of components of branch current I_1 & I_2 along X-axis
- Similarly the component of I along Y-axis is equal to the algebraic sum of component of I_1 and I_2 along Y-axis

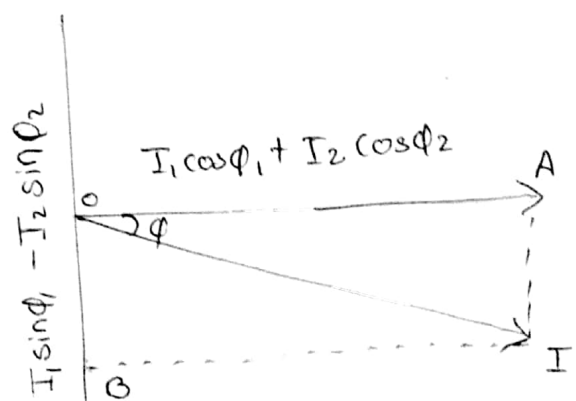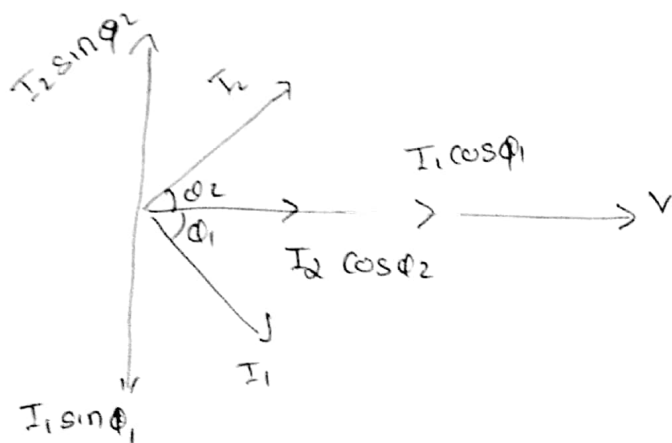

Component of resultant current along X-axis :-

= algebraic sum of I_1 and I_2 along X-axis

$$I \cos \phi = I_1 \cos \phi_1 + I_2 \cos \phi_2$$

Component of resultant current along Y-axis :-

= algebraic sum of I_1 and I_2 along Y-axis

$$I \sin \phi = I_1 \sin \phi_1 \pm I_2 \sin \phi_2$$

$$\begin{aligned} \text{Total Current } I &= \sqrt{(I \cos \phi)^2 + (I \sin \phi)^2} \\ &= \sqrt{(I_1 \cos \phi_1 + I_2 \cos \phi_2)^2 + (I_1 \sin \phi_1 \pm I_2 \sin \phi_2)^2} \end{aligned}$$

$$\tan \phi = \frac{I_1 \sin \phi_1 \pm I_2 \sin \phi_2}{I_1 \cos \phi_1 + I_2 \cos \phi_2}$$

$$\text{Phase angle } \phi = \tan^{-1} \left[\frac{I_1 \sin \phi_1 \pm I_2 \sin \phi_2}{I_1 \cos \phi_1 + I_2 \cos \phi_2} \right]$$

If $\tan \phi = \oplus$ ve current leads

If $\tan \phi = \ominus$ ve current lags

Power factor of entire circuit

$$\cos \phi = \frac{I_1 \cos \phi_1 + I_2 \cos \phi_2}{I}$$


Phasor Method :-

The reciprocal of impedance of a circuit it is called as admittance


it is represented by $Y = \frac{1}{Z} = \frac{1}{V}$

$$Y = \frac{\delta.m.s \text{ amperes}}{\delta.m.s \text{ Volts}} \quad \text{unit is Siemens "S"}$$

Inductive circuit :-

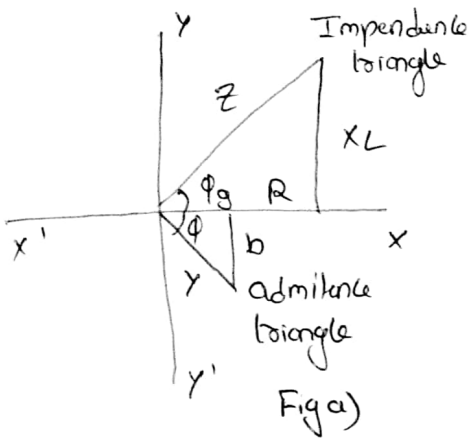

Capacitive circuit :-

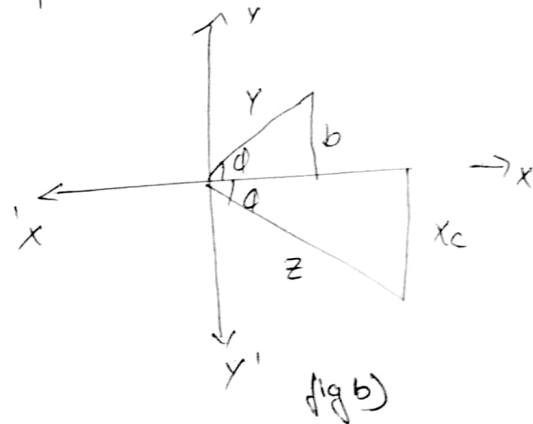

- Impedance of circuit has two rectangular components
 - Resistance " R "
 - Reactance " X "
- Admittance of circuit has two rectangular components
 - Conductance " g "
 - Susceptance " b "
- In the above figure The impedance triangle and admittance triangle.
- In the Fig a impedance and admittance triangle for inductive circuit shown it is apparent that susceptance b is negative being below X axis hence inductive susceptance is negative.
- In the Fig b impedance and admittance triangle for capacitive circuit shown it is evident that susceptance is positive, being above X axis hence capacitive susceptance is positive.

Relations :-

Conductance :- $g = Y \cos \phi$

$$g = \frac{1}{Z} \frac{R}{Z} \Rightarrow \frac{R}{Z^2} \Rightarrow \frac{R}{R^2 + X^2} \quad \text{: - Conductance is always Positive}$$

Susceptance :- $b = Y \sin \phi$

$$b = \frac{1}{Z} \frac{X}{Z} = \frac{X}{Z^2} = \frac{X}{R^2 + X^2} \quad \text{: - Susceptance } b \text{ is positive}$$

If reactance X is capacitive

: - Susceptance b is negative
If reactance X is inductive

Admittance $Y = \sqrt{g^2 + b^2}$


units of g , b and Y are in Siemens.

Application of Admittance Method :-

• let us consider a parallel circuit with 3 branches as shown

• we can determine conductance g just by adding the conductance of 3 branches

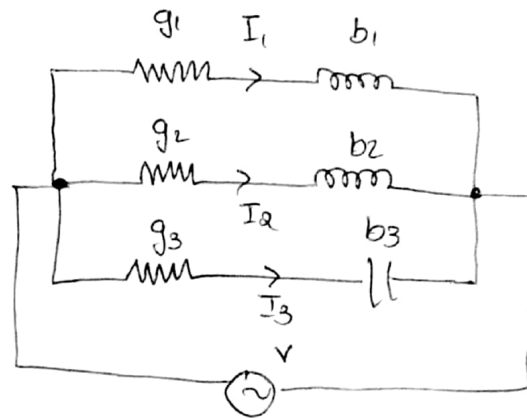• In the same way susceptance is determined by algebraic addition of susceptance of different branches.



Total conductance :- $G = g_1 + g_2 + g_3$

Total susceptance :- $B = (-b_1) + (-b_2) + b_3$

Total admittance $Y = \sqrt{G^2 + B^2}$

Total current $I = VY$

Power factor $\cos \phi = \frac{G}{Y}$

Symbolic or j Method :-


Consider parallel two-branch circuit shown in Figure with some p.d across the two impedances Z_1 and Z_2

$$I_1 = \frac{V}{Z_1} \quad \text{and} \quad I_2 = \frac{V}{Z_2}$$

$$\begin{aligned} \text{Total Current } I &= I_1 + I_2 \\ &= \frac{V}{Z_1} + \frac{V}{Z_2} \\ &= V \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) \\ &= V (Y_1 + Y_2) \end{aligned}$$

$$I = VY$$

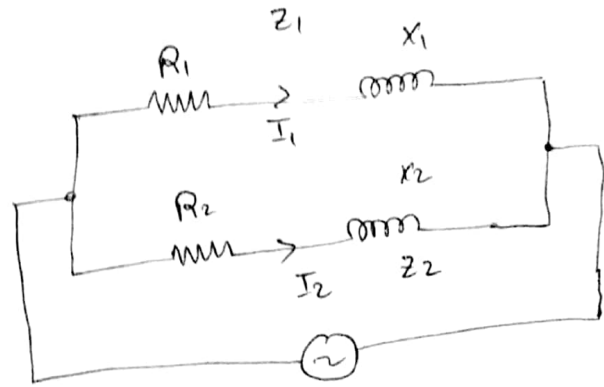where the total admittance $Y = Y_1 + Y_2$



Note :- admittances are added for parallel branches.
impedance are added for series branches.


Both admittance and impedance are complex quantities hence all addition have to be performed in complex form.

In the case of two parallel branches

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1 + jX_L} = \frac{R_1 - jX_L}{(R_1 + jX_L)(R_1 - jX_L)} = \frac{R_1 - jX_L}{R_1^2 + X_L^2} = \frac{R_1}{R_1^2 + X_L^2} - \frac{jX_L}{R_1^2 + X_L^2} = g_1 - jb_1$$

where $g_1 = \frac{R_1}{R_1^2 + X_L^2} \Rightarrow$ conductance of top branch

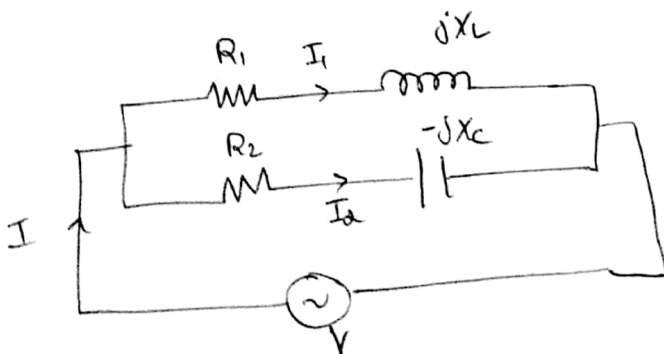$b_1 = \frac{X_L}{R_1^2 + X_L^2} \Rightarrow$ susceptance of top branch.



$$Y_2 = \frac{1}{Z_2} = \frac{1}{(R_2 - jX_C)(R_2 + jX_C)} = \frac{R_2 + jX_C}{R_2^2 + X_C^2}$$

$$\Rightarrow \frac{R_2 + jX_C}{R_2^2 + X_C^2} = \frac{R_2}{R_2^2 + X_C^2} + \frac{jX_C}{R_2^2 + X_C^2}$$

$$= g_2 + jb_2$$

∴ Total admittance $Y = Y_1 + Y_2$
 $= (g_1 - jb_1) + (g_2 + jb_2)$
 $= (g_1 + g_2) - j(b_1 - b_2)$
 $Y = G - jB$

$$Y = \sqrt{(g_1 + g_2)^2 + (b_1 - b_2)^2}$$

$$\phi = \tan^{-1} \left[\frac{b_1 - b_2}{g_1 + g_2} \right]$$

∴ In Polar form, admittance $Y = Y \angle \phi^\circ$

$$Y = \sqrt{G^2 + B^2} \angle \tan^{-1} \left(\frac{B}{G} \right)$$

∴ Total Current $I = YV$

$$I_1 = VY_1$$

$$I_2 = VY_2$$

$$V = V \angle 0^\circ \text{ and } Y = Y \angle \phi$$

$$I = VY$$

$$V \angle 0^\circ \times Y \angle \phi = VY \angle \phi$$

∴ Considering general case ∴

$$V = V \angle \alpha$$

$$Y = Y \angle \beta$$

$$I = VY$$

$$= V \angle \alpha \times Y \angle \beta = VY \angle \alpha + \beta$$