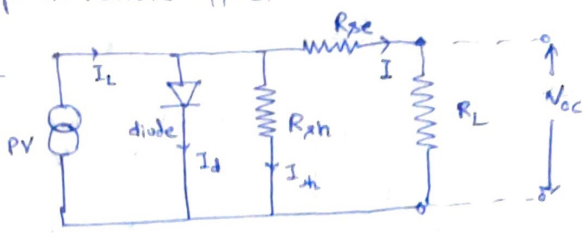


Equivalent Circuit of Solar Cell
Figure of merits of Solar Cell

Principle of solar cell is photovoltaic effect.....

Figure of merits of solar cell:-

Eq ckt of solar cell:-



- In presence of illumination

An absence of illumination

$$I_d = I_0 \left\{ e^{\frac{q(V - I R_{sh})}{nKT}} - 1 \right\}$$

$$I = I_L \left\{ e^{\frac{q(V - I R_{sh})}{nKT}} - 1 \right\} - I_L \frac{V - I R_{sh}}{R_{sh}}$$

Figure of Merit of Solar Cell →


- (i) Short ckt current (I_{sc})
- (ii) Open ckt voltage (V_{oc})
- (iii) Curve Factor or Fill Factor (FF)
- (iv) Efficiency
- (v) diode ideality factor
- (vi) Parasite Resistance.

(i) Short ckt current (I_{sc})

Considering shunt resistor $R_{sh} \approx 100 \Omega$, then $\frac{V - I R_{sh}}{R_{sh}} \rightarrow 0$

$$I = I_0 \left\{ e^{\frac{q(V - I R_{sh})}{nKT}} - 1 \right\} - I_L$$

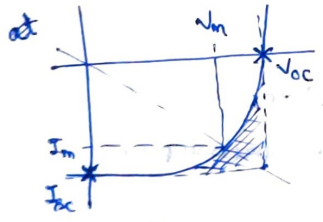where I_0 → Reverse Sat current
 k → Boltzman Const.
 n → diode ideality factor
 T → Temp in K
 I_L → Light generated current



At $V=0$, $I = I_{sc}$

$$I_{sc} = I_0 \left\{ e^{\frac{-q I_{sc} R_{sh}}{nKT}} - 1 \right\} - I_L \therefore I_{sc} \approx -I_L$$

(ii) Fill Factor = degree of squareness of I-V curve

$$= \frac{V_m I_m}{V_{oc} I_{sc}}$$

(ii) Open ckt Voltage (V_{oc})

At $I=0$, $V = V_{oc}$

$$0 = I_0 \left\{ e^{\frac{q V_{oc}}{nKT}} - 1 \right\} - I_L$$

$$\therefore e^{\frac{q V_{oc}}{nKT}} = 1 + \frac{I_L}{I_0} \quad \text{or}$$

$$\text{or } V_{oc} = \frac{nKT}{q} \ln \left(\frac{I_L}{I_0} \right) \Rightarrow V_{oc} = \frac{nKT}{q} \ln \left(\frac{I_{sc}}{I_0} \right)$$

(iv) Efficiency (η)

$$= \frac{\text{Output}}{\text{Input}} = \frac{I_m V_m}{\text{Cell Area} \times \text{Power Input}} \times 100\%$$

$$= \frac{I_{sc} V_{oc}}{A \times P_m} \times FF \times 100\%$$

from solar radiation dt.


Now $I_{sc} \propto I_{int}$
 $V_{oc} \propto \ln(k I_{int})$

$$I_0 \sim 10^{-6} \text{ A} \therefore \frac{I_L}{I_0} \gg 1 \quad I_L \approx I_{sc}$$

⑤ diode ideality factor n or A

$$A = \frac{V_1 - V_2}{25 \times 10^{-3} \ln(I_1/I_2)}$$

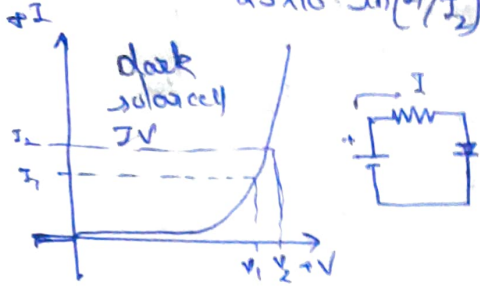where I_1, I_2, V_1, V_2 are respective voltage & current at diff pts during dark calib.



In dark conditions

$$I = I_0 \left\{ e^{\frac{q(V - IR_s)}{AKT}} - 1 \right\}$$

$\therefore V \gg IR_s$ & V is very high

$$\therefore I = I_0 e^{\frac{qV}{AKT}}$$

$$\therefore \frac{I_1}{I_2} = e^{\frac{q}{AKT}(V_1 - V_2)}$$

$$\therefore (V_1 - V_2) \times \frac{q}{AKT} = \ln\left(\frac{I_1}{I_2}\right) \Rightarrow A = \frac{V_1 - V_2}{\ln(I_1/I_2)} \left(\frac{q}{KT}\right)$$

now at $T = 300 \text{ K}$, $\frac{KT}{q} = 0.025$ $\therefore A = \frac{V_1 - V_2}{\ln(I_1/I_2) \times 25 \times 10^{-3}}$

⑥ Parasitic Resistances :- (R_s & R_{sh})

R_s has great influence on I_{sc} & FF
 R_{sh} has min influence on V_{oc}

In real cells power is dissipated through the resistance of the contacts &

leakage resistance of diode. These are effects are equivalent to a parasitic R_s & R_{sh}

R_s arises from resistance of the cell material to current flow, particularly through the front surface to the contact & from resistive contacts. Series resistance is a particular problem at high current densities, for instance under concentrated light.

R_{sh} arises from leakage of current through the cell, around the edge of the device & bet the contacts of diff polarity. It is a prob in poor rectifying devices.

Both R_s & R_{sh} have big impact on cell performance. Both of them reduce FF & ultimately η .

R_s to be kept as low as possible & R_{sh} as \uparrow as possible