



**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**List of Experiments:**

1. Characteristics of Fluorescent lamp
2. Characteristics of Tungsten & Carbon Filament lamp
3. Verification of Superposition Theorem
4. Verification of Thevenin's Theorem
5. Verification of Norton's Theorem
6. Calibration of Ammeter & Voltmeter
7. Starting & Reversing of DC shunt motor
8. Study of series RLC circuit
9. Calibration of Energy meter
10. Y- $\Delta$  relation of 3-phase Electrical Network
11. OC and SC test of 1-phase transformer




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 1

**Title:** Characteristics of Fluorescent lamp

**Objective:** To understand the operation and characteristics of fluorescent lamp

**Circuit Diagram:**

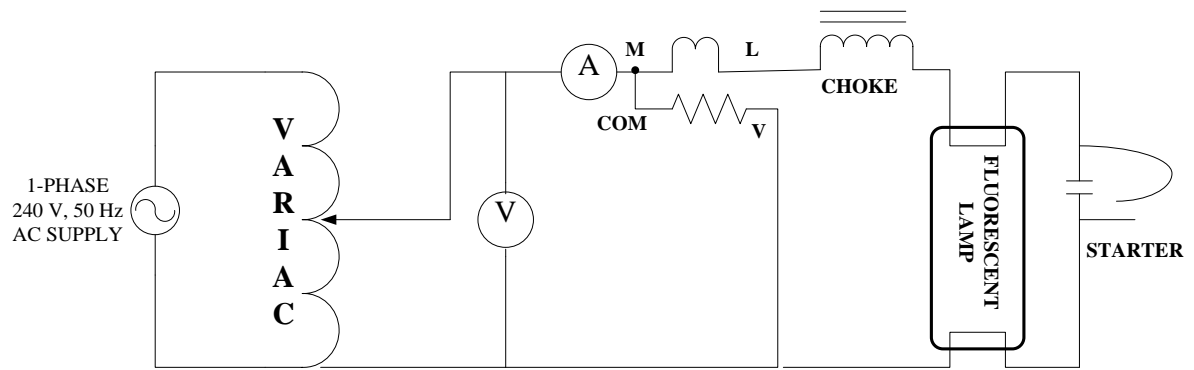

Circuit diagram for Fluorescent Lamp

**Data Table**

Sl no	Increasing Voltage				Decreasing Voltage			
	Striking Voltage=				Cut-off voltage=			
	Supply voltage in V	Current in A	Power in W	Power factor $\cos \phi = W/(V \times I)$	Supply voltage in V	Current in A	Power in W	Power factor $\cos \phi = W/(V \times I)$
1								
2								
3								
4								
5								
6								

**Discussion**

1. Plot Power factor versus Voltage curve
2. Explain role of starter and choke

Student Name:

Signature of the teacher

Student Roll No:

Signature:




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 2

**Title:** Characteristics of Tungsten & Carbon filament lamp

**Objective:** To understand the working & characteristics of Tungsten & Carbon filament lamps as well as their nature of resistivity.

**Circuit Diagram:**

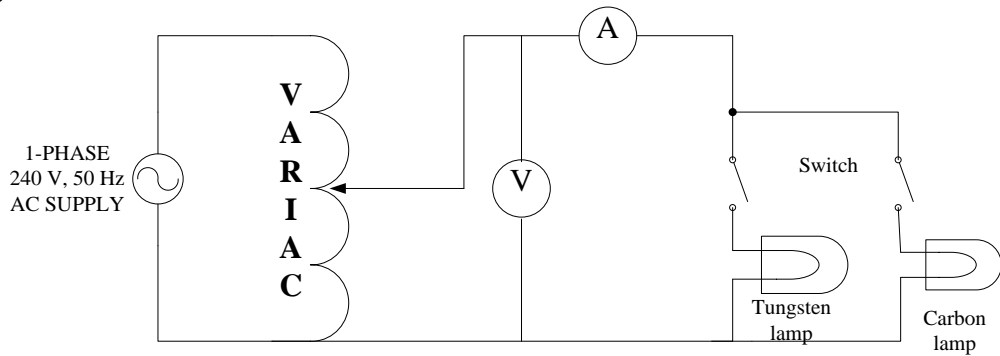

**Circuit diagram for Tungsten, Carbon filament lamp**

**Data Table:**

Sl no	Tungsten lamp			Carbon lamp		
	Voltage (V)	Current (A)	Impedance ( $\Omega$ )	Voltage (V)	Current (A)	Impedance ( $\Omega$ )
1						
2						
3						
4						
5						
6						
7						
8						
9						
10						

**Discussion**

1. Plot Impedance v Voltage curve for both the lamps
2. Discuss the difference between two lamps

Student Name:  
 Student Roll No:  
 Signature:

Signature of the teacher



**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 3

**Title:** Verification of Superposition theorem

**Objective:** To verify the superposition theorem for linear responses in a multisource DC circuit

**Circuit Diagram:**

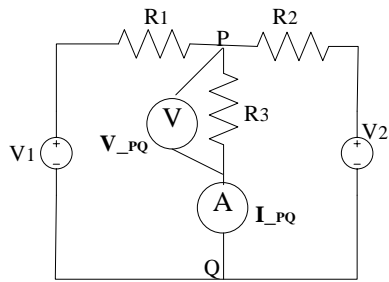


Fig 1

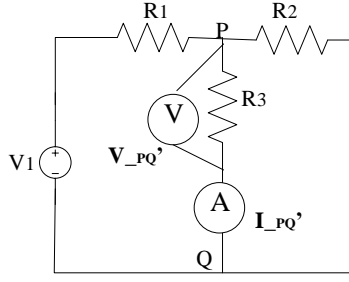


Fig 2

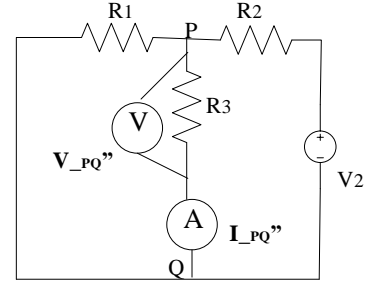


Fig 3

Circuit diagram for verification of Superposition theorem

**Data Table**

**V1 =**           , **V2 =**           , **R1 =**           , **R2 =**           , **R3 =**

$V_{PQ}$	$I_{PQ}$	$V_{PQ}'$	$I_{PQ}'$	$V_{PQ}''$	$I_{PQ}''$	$V_{PQ}' + V_{PQ}''$	$I_{PQ}' + I_{PQ}''$

**V1 =**           , **V2 =**           , **R1 =**           , **R2 =**           , **R3 =**

$V_{PQ}$	$I_{PQ}$	$V_{PQ}'$	$I_{PQ}'$	$V_{PQ}''$	$I_{PQ}''$	$V_{PQ}' + V_{PQ}''$	$I_{PQ}' + I_{PQ}''$

**V1 =**           , **V2 =**           , **R1 =**           , **R2 =**           , **R3 =**

$V_{PQ}$	$I_{PQ}$	$V_{PQ}'$	$I_{PQ}'$	$V_{PQ}''$	$I_{PQ}''$	$V_{PQ}' + V_{PQ}''$	$I_{PQ}' + I_{PQ}''$

**Discussion:**

Calculate current flowing through and voltage across  $R_3$  using theoretical calculations.

Student Name:

Signature of the teacher

Student Roll No:

Signature:




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 4


**Title:** Verification of Thevenin's theorem

**Objective:** To verify the Thevenin's Theorem in a linear DC circuit.


**Circuit Diagram:**

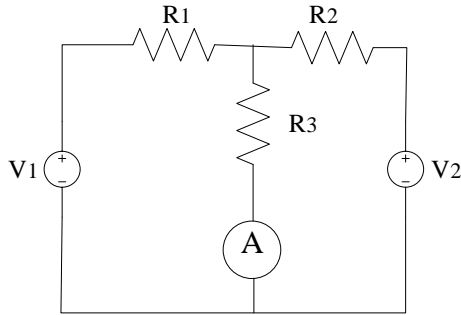


**Fig 1**

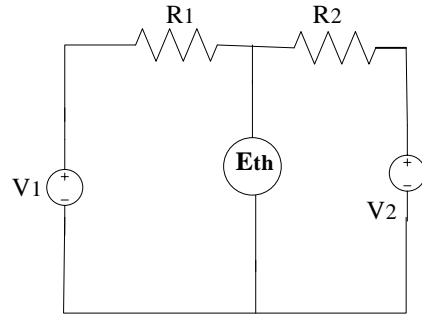

**Fig 2**

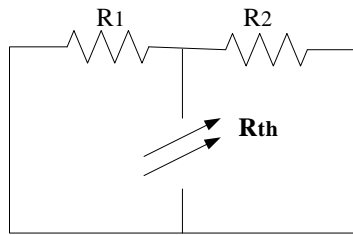

**Fig 3**

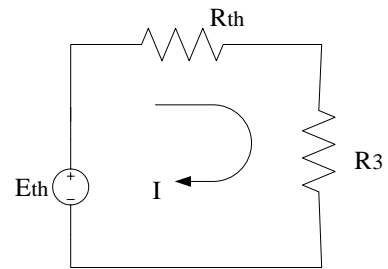

**Fig 4**

**Circuit diagram for verification of Thevenin's theorem**

**Data table**

$V_1 =$	<b>As per Fig 1:</b> $I_{measured} =$	<b>Verification</b> <b>As per Fig 4</b> $I_{verified} = E_{th} / (R_{th} + R_3)$	% Error = $100 \times (I_{measured} - I_{verified}) / I_{measured}$
$V_2 =$			
$R_1 =$	<b>As per Fig 2:</b> $E_{th} =$		
$R_2 =$			
$R_3 =$			

**Discussion:**

Verify all steps through theoretical calculations.

Student Name:  
 Student Roll No:  
 Signature:

Signature of the teacher




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 5


**Title:** Verification of Norton's theorem

**Objective:** To verify the Norton's Theorem in a linear DC circuit


**Circuit Diagram:**

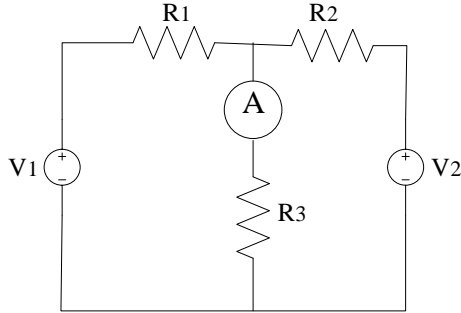


**Fig 1**

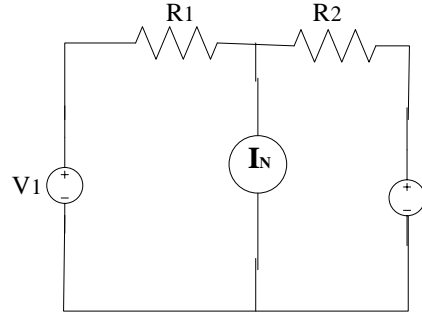

**Fig 2**

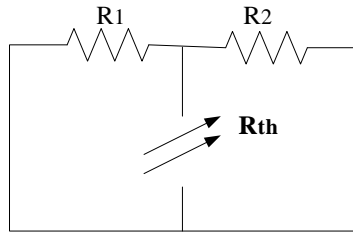

**Fig 3**

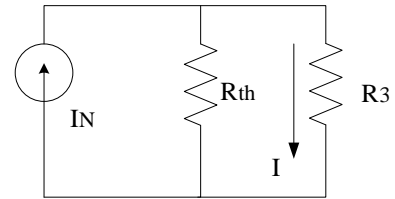

**Fig 4**

**Circuit diagram for verification of Norton's theorem**

**Data table:**

$V_1 =$	<b>As per Fig 1:</b> $I_{measured} =$	<b>Verification</b> <b>As per Fig 4</b> $I_{verified} = \frac{(I_N \times R_{th})}{(R_{th} + R_3)}$	% Error = $100 \times (I_{measured} - I_{verified}) / I_{measured}$
$V_2 =$			
$R_1 =$	<b>As per Fig 2:</b> $I_N =$		
$R_2 =$			
$R_3 =$			

**Discussion:**

Verify all steps through theoretical calculations.

Student Name:  
 Student Roll No:  
 Signature:

Signature of the teacher




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 6

**Title:** Calibration of Ammeter & Voltmeter

**Objective:** To find the error in measurement in test meters by checking them against standard meters.

**Circuit Diagram:**

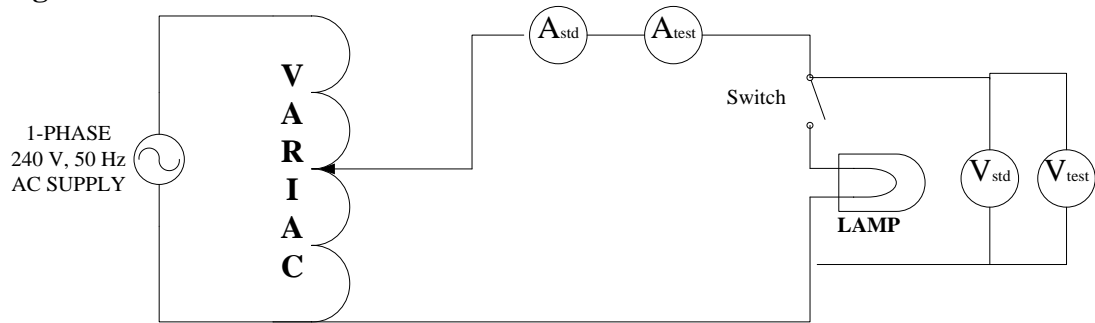

**Circuit diagram for Calibration of Ammeter & Voltmeter**

**Data Table:**

Sl no	Standard Voltage in V ( $V_{std}$ )	Test Voltage in V ( $V_{test}$ )	% Error = $(100 \times (V_{std} - V_{test})/V_{test})$	Standard Current in A ( $I_{std}$ )	Test Current in I ( $I_{test}$ )	% Error = $(100 \times (I_{std} - I_{test})/I_{test})$
1						
2						
3						
4						
5						
6						
7						

**Discussion**

Plot (I) Error versus  $I_{test}$ , (II) Error versus  $V_{test}$ .

Student Name:

Signature of the teacher

Student Roll No:

Signature:




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 7

**Title:** Starting & Reversing of DC shunt motor

**Objective:** To learn about the starter(s) of a DC motor as well as see its working. Also, learn about the effect of various terminals changes on the direction of the DC motor.

**Circuit Diagram:**

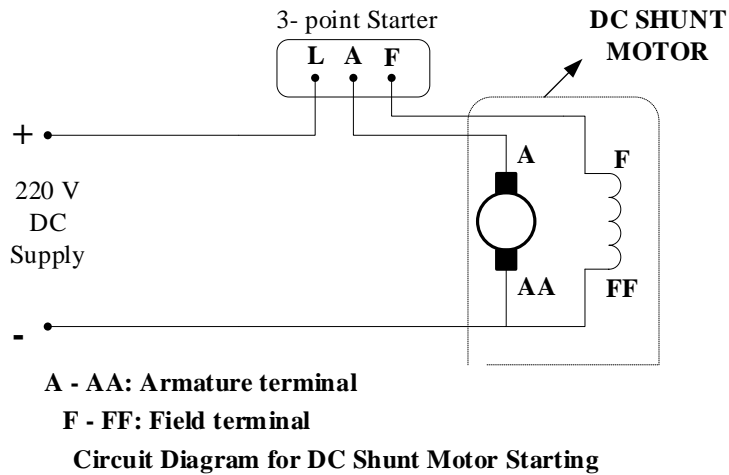

**Data Table:**

Scheme	Direction of Rotation (CW/CCW)	Speed in rpm
Original		
Armature is reversed		
Field is reversed		
Armature & Field both are reversed		
Supply terminal is reversed		

**Discussion**

Explain Function of 3-point starter.

Student Name:  
 Student Roll No:  
 Signature:

Signature of the teacher






**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 8

**Title:** Study of Series RLC circuit

**Objective:** To find the values of Resistance, Inductance, Capacitance, Inductor internal resistance and power factor of a series RLC circuit

**Circuit Diagram:**

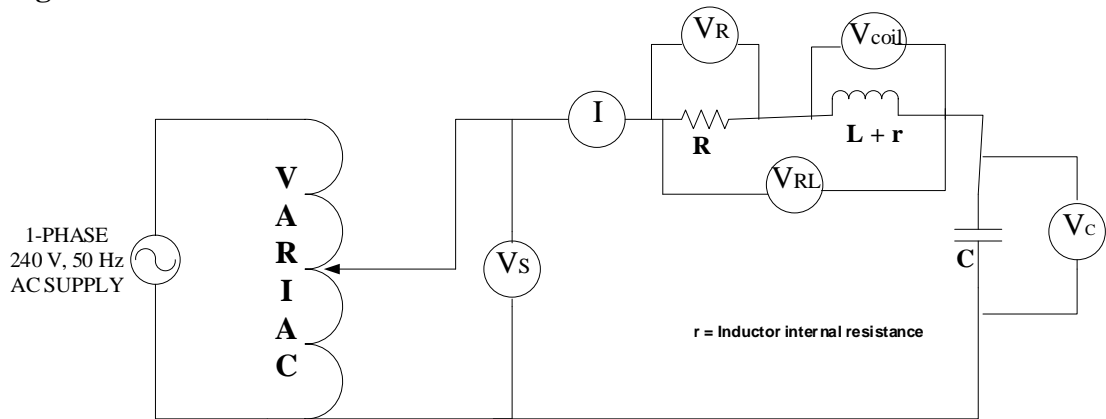

Circuit diagram of Series RLC circuit

**Data Table:**

Sl no	V <sub>s</sub> (V)	I (A)	V <sub>R</sub> (V)	V <sub>coil</sub> (V)	V <sub>RL</sub> (V)	V <sub>c</sub> (V)
1						
2						
3						
4						
5						

$$r = \frac{Z_{RL}^2 - Z_{coil}^2 - R^2}{2R}$$

$$X_L = \frac{R^2 + X_C^2 + Z_{coil}^2 + 2Rr - Z^2}{2X_C}$$

**Calculation Table: (use appropriate units)**

Z = V <sub>s</sub> /I	Z <sub>coil</sub> = V <sub>coil</sub> /I	Z <sub>RL</sub> = V <sub>RL</sub> /I	R = V <sub>R</sub> /I	X <sub>c</sub> = V <sub>C</sub> /I	C = 1/(2ΠfX <sub>C</sub> )	r	X <sub>L</sub>	L = X <sub>L</sub> /(2Πf)	PF = (R+r)/Z

**Discussion:**

Draw phasor diagram of series RLC circuit

Student Name:

Signature of the teacher

Student Roll No:

Signature:




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 9

**Title:** Calibration of Energy meter

**Objective:** To familiarize with the analog type energy meter and find the discrepancy in measurement of power (energy) by different methods.

**Circuit Diagram:**

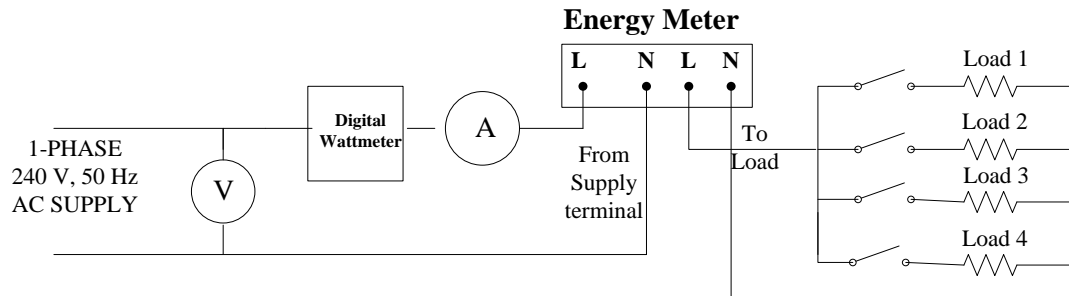

**Circuit diagram for Calibration of Energy meter**

**Data Table:**

**Time=**

Voltage in V	Current in A	Power $V \times I$ ( $W_c$ )	Power ( $W_m$ )	% error in Power	$E_c = W_m \times t$	Energy ( $E_m$ )	% error in Energy

**Discussion:**

Explain what is creeping

Student Name:

Signature of the teacher

Student Roll No:

Signature:




**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 10

**Title:** Y-Δ relation of 3-phase Electrical Network

**Objective:** To verify the relations among phase and line quantities of different three-phase connections.

**Circuit Diagram:**

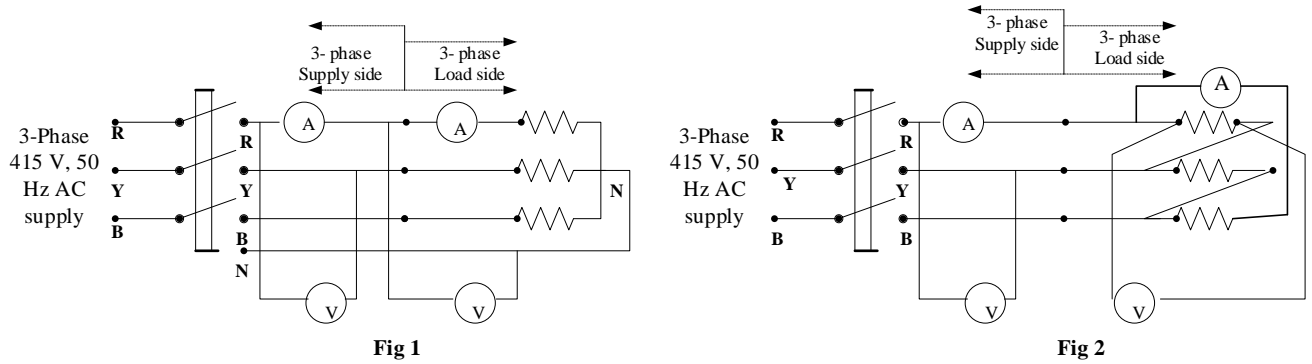

Circuit diagram for 3-phase Electrical Network

**Data table:**

Sl no	Y- Network (Fig 1)						Δ- Network (Fig 2)					
	Line Voltage in V	Line Current in A	Phase Voltage in V	Phase Current in A	$V_{Ph}/V_L$	$I_{Ph}/I_L$	Line Voltage in V	Line Current in A	Phase Voltage in V	Phase Current in A	$V_{Ph}/V_L$	$I_{Ph}/I_L$
1												
2												
3												
4												
5												
6												

**Discussion:**

Derive the relation between  $V_{line}$  and  $V_{phase}$  and  $I_{line}$  and  $I_{phase}$  for Y and Δ network.

Student Name:  
 Student Roll No:  
 Signature:

Signature of the teacher





**Electrical Engineering Department**  
**Basic Electrical Engineering Laboratory**  
**EENUGES02**

**Experiment no:** 11

**Title:** Open circuit and Short circuit test of 1- phase transformer

**Objective:** To calculate various parameters of 1- phase transformer

**Circuit Diagram:**

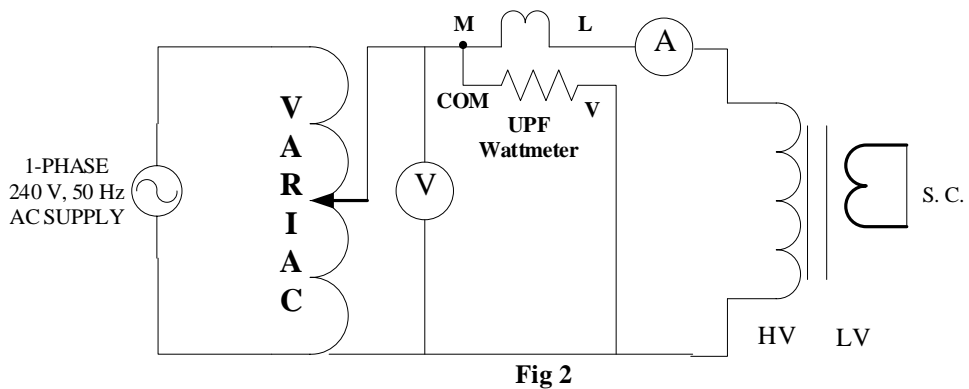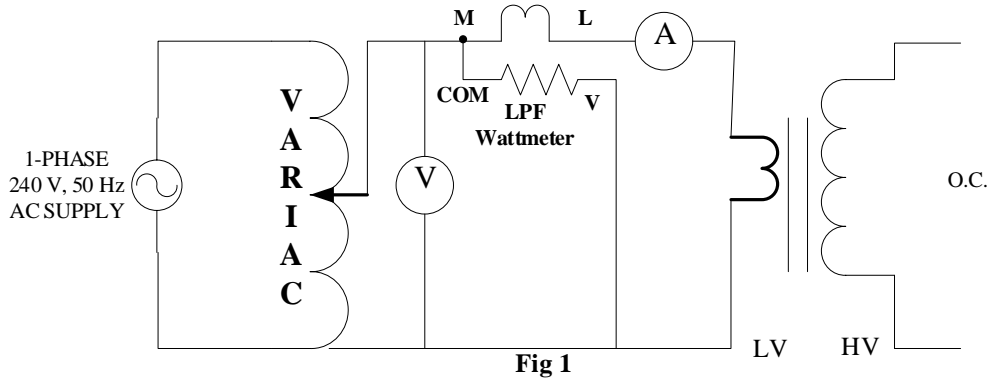

**Circuit Diagrams for O.C. & S. C. Test of 1-phase Transformer**

**Data Table:**

<b>OPEN CIRCUIT TEST (Fig 1)</b>			<b>SHORT CIRCUIT TEST (Fig 2)</b>		
Voltage in (V)	Current in (A)	Power in (W)	Voltage in (V)	Current in (A)	Power in (W)

**Discussion:**

Evaluate parameters of 1- phase transformer

Student Name:

Student Roll No:

Signature:

Signature of the teacher